

LOSS LESS TRANS. LINE




-Dr. Pranjal Saxena

(Assistant Professor)

B.Tech, M.Tech, PhD

techinsight08@gmail.com



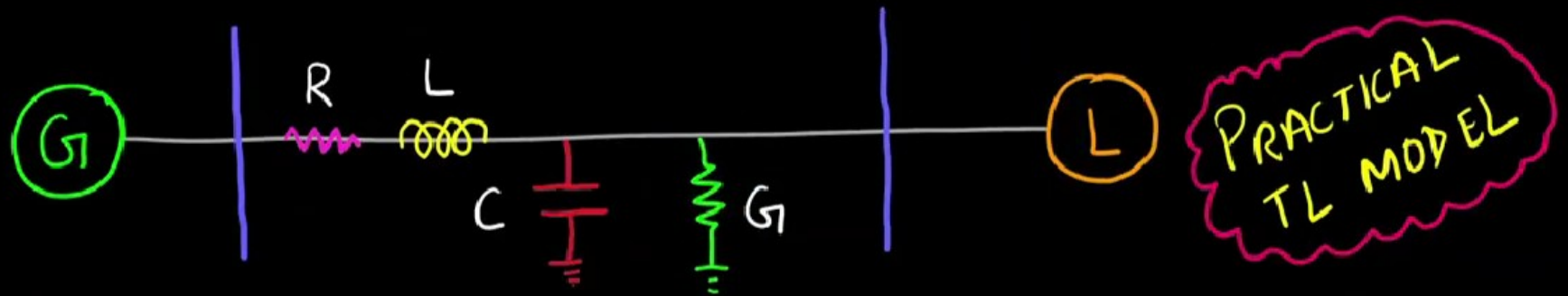



* $\text{---} \text{ } R \text{ ---}$ \rightarrow Losses in conductor \rightarrow Lossy conductor

$\text{---} \text{ } G \text{ ---}$ \rightarrow Losses in dielectric \rightarrow Lossy insulator

* Ideal TL \rightarrow Losses = 0 \rightarrow $R=0, G=0$ \rightarrow **LOSSLESS TL**

Lossless Transmission Line

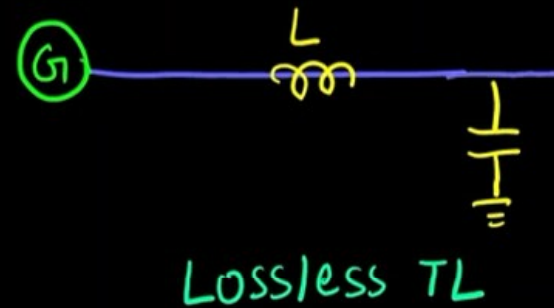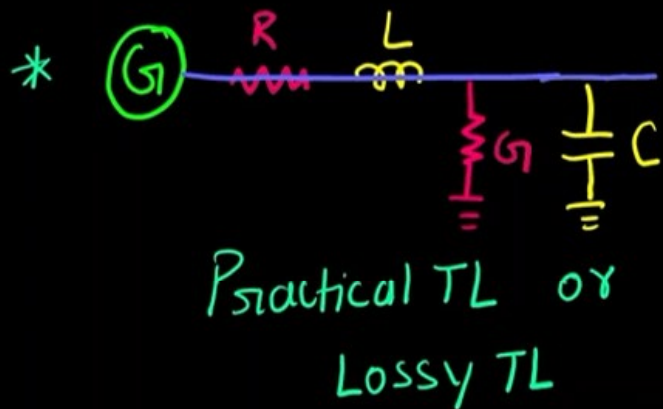
"A TL that only exhibit pure reactive component (L, C) and zero loss component ($R = G = 0$)."



* Ideal Lossless line $\rightarrow R = 0, G = 0$


Practical lossless line $\rightarrow R \ll \omega L, G \ll \omega C$

Features of Lossless TL

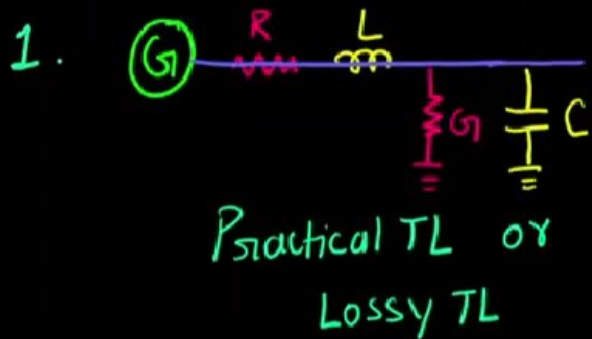

$$Z(\text{series impedance}) = R + j\omega L$$
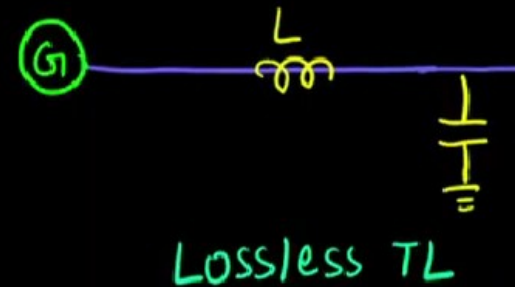
$$Y(\text{shunt admittance}) = G + j\omega C$$



$$Z = j\omega L \quad [R \ll j\omega L]$$

$$Y = j\omega C \quad [G \ll j\omega C]$$

2. In lossless line,

$$P_{\text{delivered}} = P_{\text{Received}}$$

→ No power loss b/w source and Load end


3. In lossless TL

└→ Line conductors → Perfect Conductor
└→ Dielectric → Perfect Insulator

4.

TL Nature	Line Parameters	Surge Impedance	Z_0 Nature
Lossy	R, L, C, G	$\sqrt{\frac{R + j\omega L}{G + j\omega C}}$	complex
Lossless	L, C	$\sqrt{L/C}$	Real

5. Attenuation Constant (α)

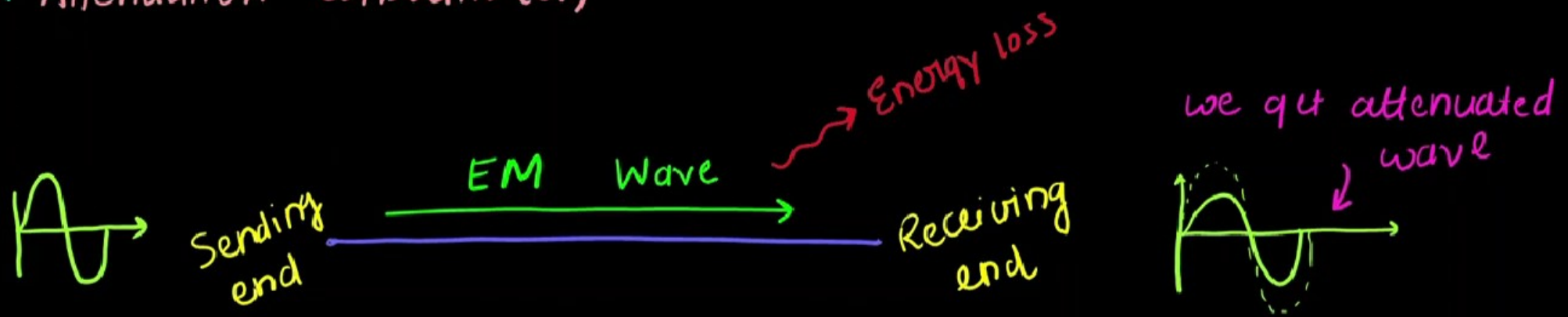

attenuation constant : measure attenuation of EM wave
(α)
passing through a **medium**

* wave attenuation
 R, G
of TL

Lossy
 $\alpha \neq 0$

Lossless
 $\alpha = 0$

6. We know that Lossless line is physically Impossible



Practical Importance?
→ use loss line TL equations
to approximate the behavior
of low-Loss TL.

SURGE IMPEDANCE



-Dr. Pranjal Saxena

(Assistant Professor)

B.Tech, M.Tech, PhD

techinsight08@gmail.com



Surge Impedance

"In a lossless line, the impedance offer by line Inductance and Capacitance is known as **Surge impedance**"




* Surge impedance also known as;

- characteristic impedance
- Natural impedance

Meaning

1. Surge impedance →

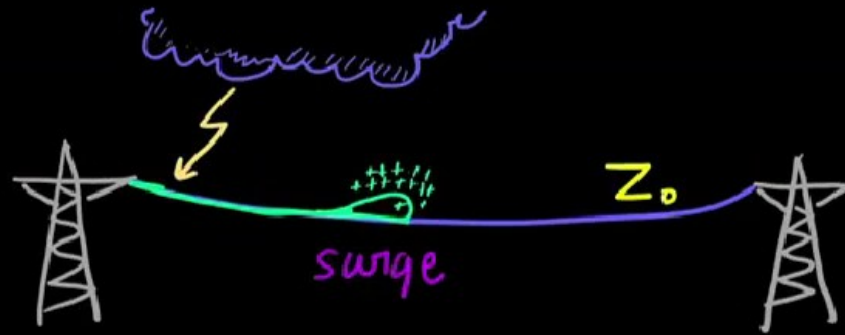

“Impedance that will offer by TL to the surge flowing through it”

2. Natural Impedance

“surge impedance has nothing to do with load, Z_0 is natural impedance offered the TL.”

3. Characteristic impedance → as it is decided by the geometry of 2 conductors.

Features of Surge Impedance

* Z_0 (Over Head TL) \longrightarrow 400 to 600 Ω

Z_0 (underground)
Cable \longrightarrow 40 to 60 Ω

\hookrightarrow As cable has 20 to 60 times more capacitance than OHTL


* Surge impedance $= \sqrt{\frac{L}{C}}$ \longrightarrow independent of Length
 \longrightarrow depends on spacing b/w conductors

* Value of surge impedance will be same at all pts of line




Calculation of characteristic Impedance

①
2-conductor
TL

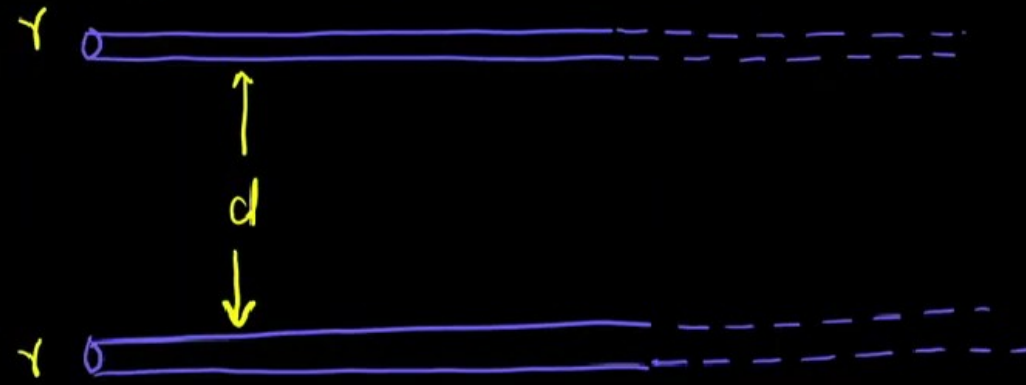


$$Z_0 = \frac{276}{\sqrt{\epsilon_r}} \log \frac{d}{r}$$


②
Coaxial
cable

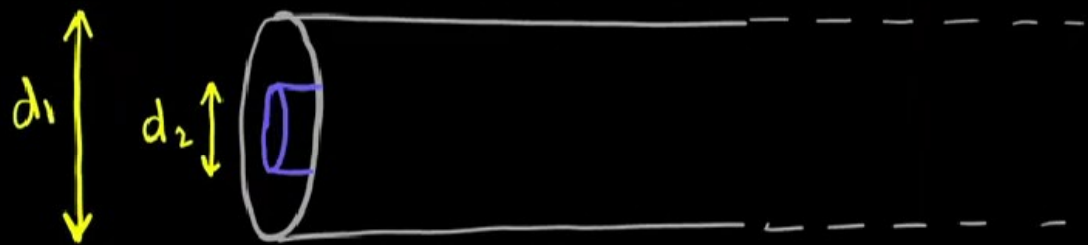
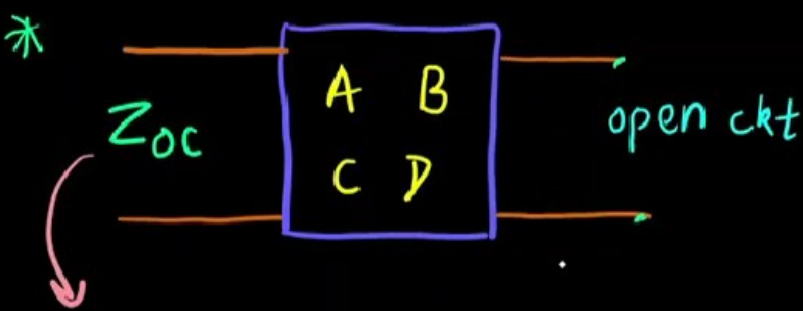
$$Z_0 = \frac{138}{\sqrt{\epsilon_r}} \log \frac{d_1}{d_2}$$



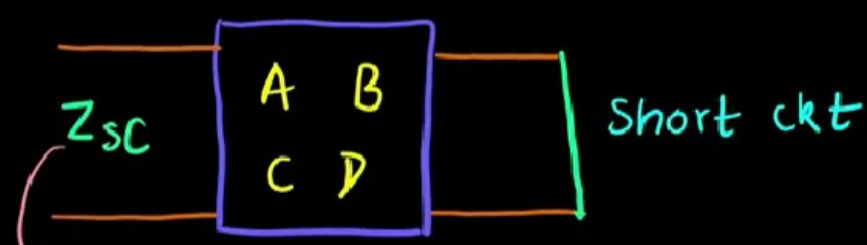open ckt impedance $\rightarrow \frac{1}{C}$



short ckt impedance $\rightarrow B$

$\rightarrow Z_{oc} \cdot Z_{sc} = \frac{B}{C} = \frac{Z}{Y}$

\nearrow series impedance
 \nwarrow shunt admittance

$\rightarrow Z_0 = \sqrt{Z_{oc} \cdot Z_{sc}} = \sqrt{\frac{B}{C}} = \sqrt{\frac{Z}{Y}}$

A	V_s/V_R	Voltage Ratio or Reverse Voltage gain	No unit
B	V_s/I_R	Short Circuit Resistance or Reverse transfer impedance	ohm
C	I_s/V_R	Open circuit conductance or Reverse transfer admittance	mho
D	I_s/I_R	Current Ratio or Reverse current gain	No unit



SURGE IMPEDANCE LOADING





-Dr. Pranjal Saxena

(Assistant Professor)

B.Tech, M.Tech, PhD


techinsight08@gmail.com



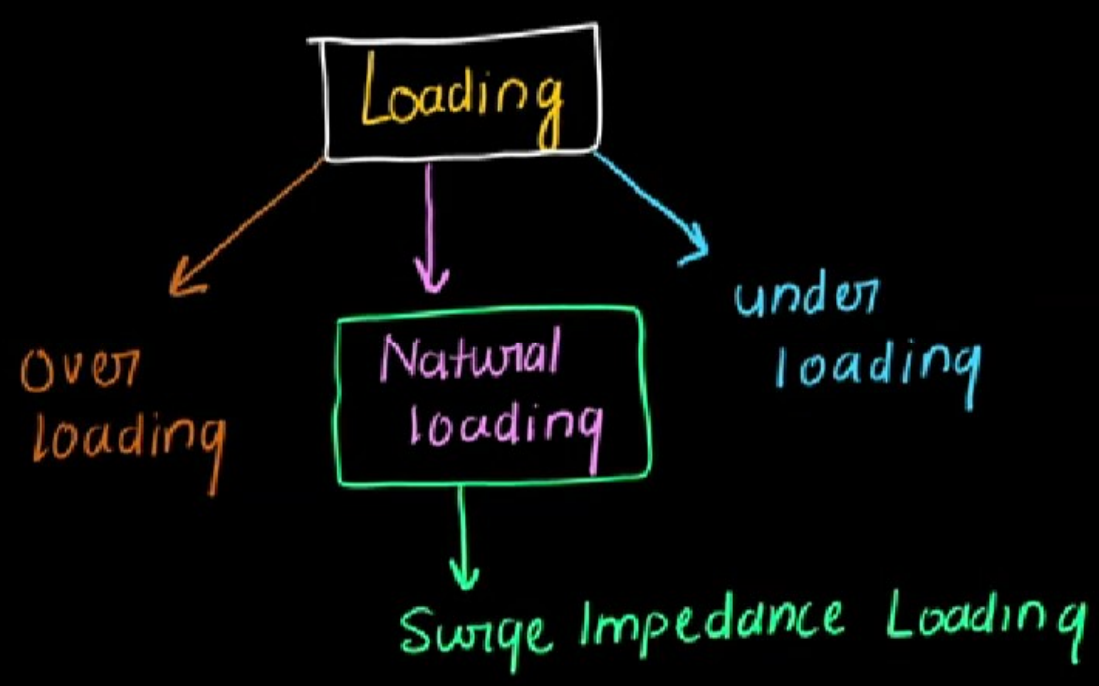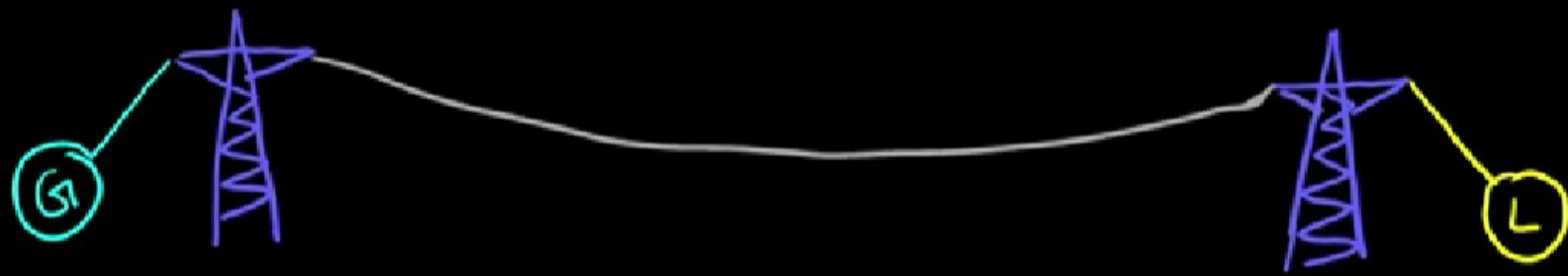

Surge Impedance Loading

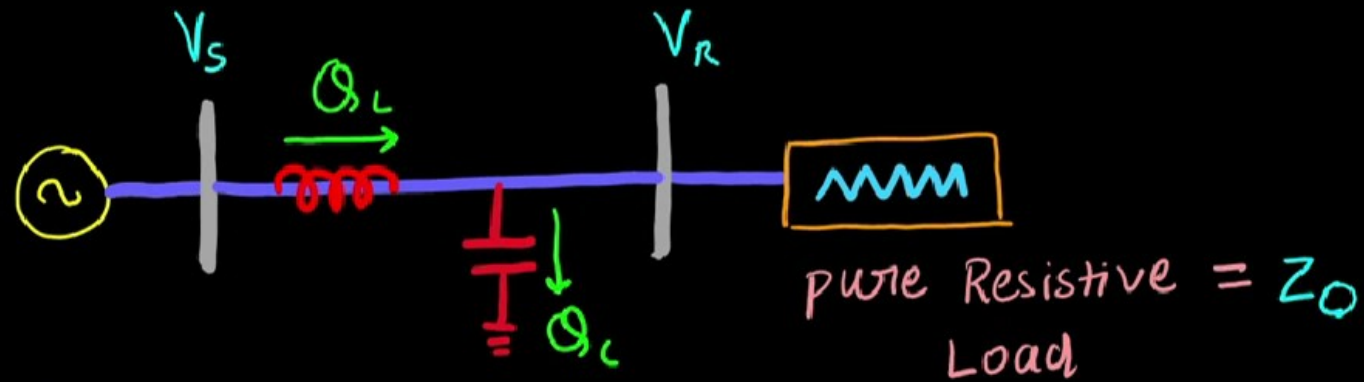"SIL is the power delivered by the TL to a purely resistive load equal to its surge impedance."



* In surge impedance loading

$$\rightarrow Q_L = Q_c \rightarrow V_s = V_R$$

* Called natural loading

$$\therefore \boxed{SIL = \frac{V_R^2}{Z_0}} \quad \text{W or MW}$$

Calculating Surge Impedance

* $Q_L = Q_C \rightarrow$ Surge loading conditions

$$Q_C = Q_L$$

$$\frac{V_\phi^2}{X_C} = I_\phi^2 X_L$$

$$\frac{V}{I} = \sqrt{X_L X_C} = \sqrt{\frac{j\omega L l}{j\omega C l}} = \sqrt{\frac{L}{C}}$$

$$\therefore \boxed{Z_0 = \sqrt{\frac{L}{C}}}$$

Importance of SIL


* Help in determining the max^m loading of TL

Loading Conditions	Voltage	Profile
Loading $>$ SIL	$V_R < V_S$	Sag
Loading $=$ SIL	$V_R = V_S$	Flat
Loading $<$ SIL	$V_R > V_S$	Swell

(Ferranti Effect)



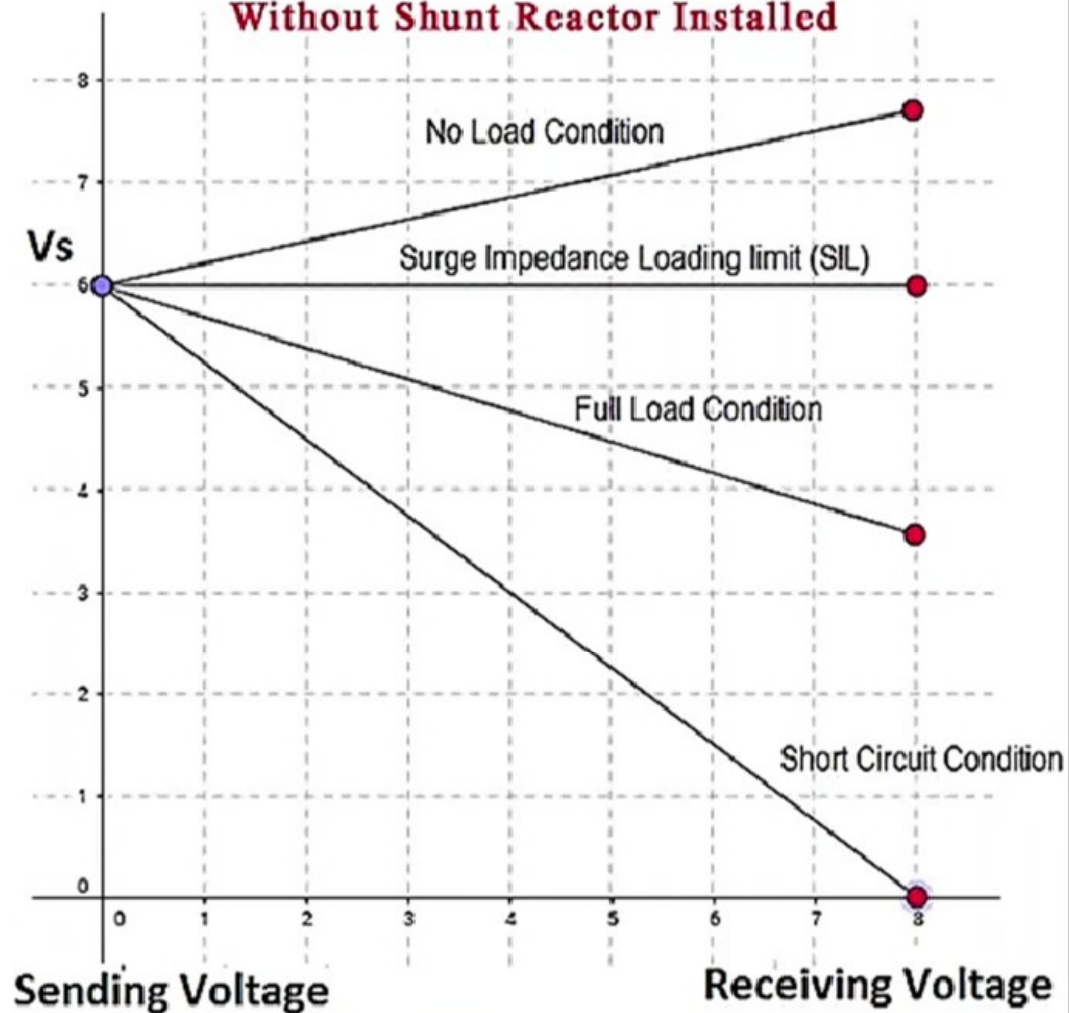Voltage Behavior of a Long Transmission Line Without Shunt Reactor Installed





High Capacitance

↓
 Z_0 ↓

↓
SIL ↑



More power can be
transfer without overload.

Low capacitance

↓
 Z_0 ↑

↓
SIL ↓



Less power can
be transfer without
overload.

NOTE → High value of Z_0 is undesirable.