

# STRING EFFICIENCY



**-Dr. Pranjal Saxena**


(Assistant Professor)

**B.Tech, M.Tech, PhD**

[techinsight08@gmail.com](mailto:techinsight08@gmail.com)




# # Capacitor model of Insulator string

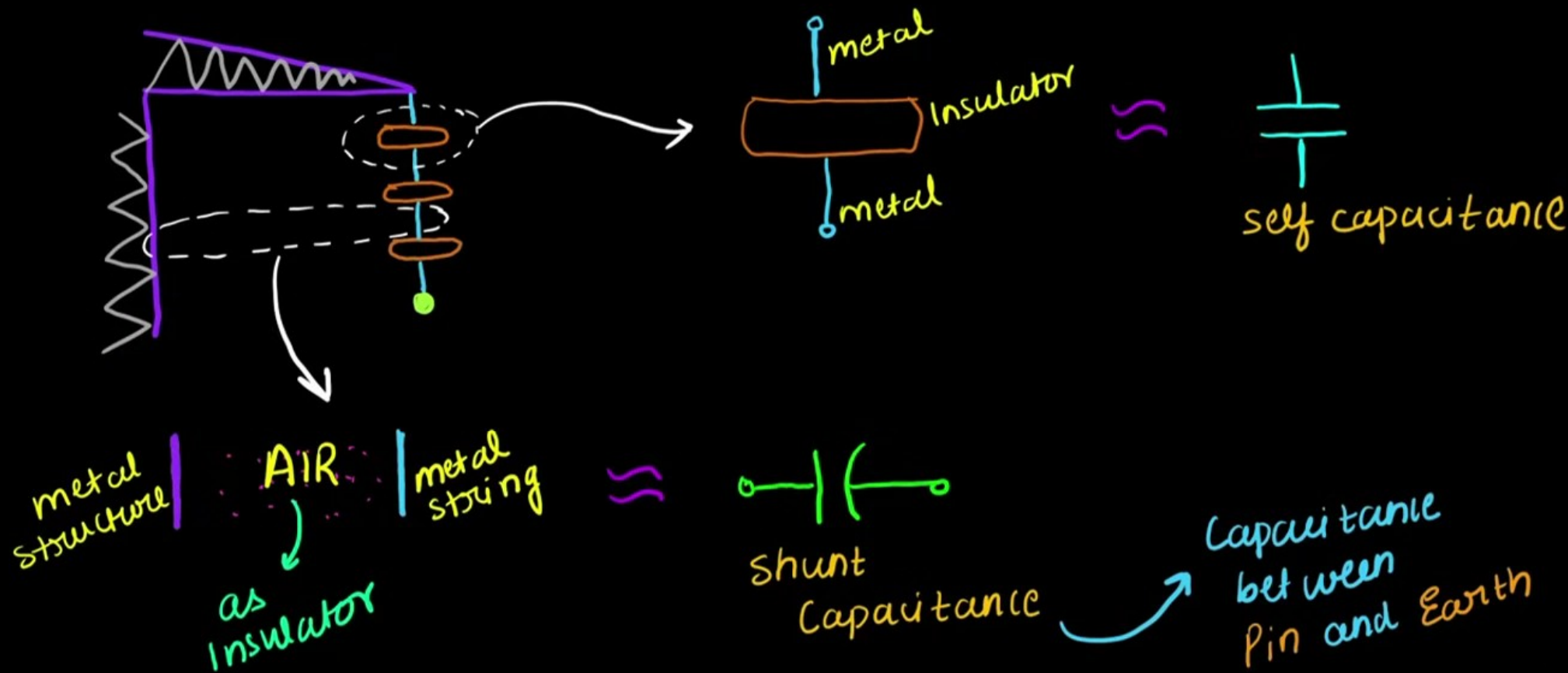

# # Voltage distribution


Ideally

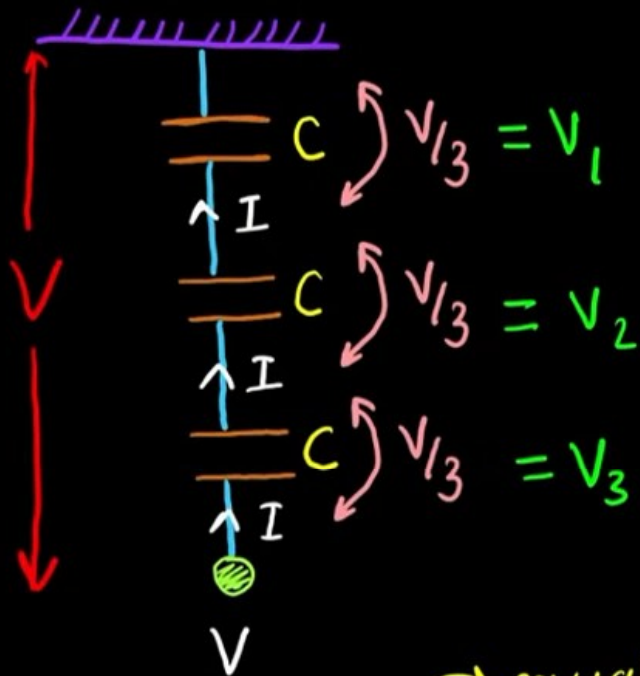

$$V_1 = V_2 = V_3$$

equal  
distribution  
of voltage

Practically

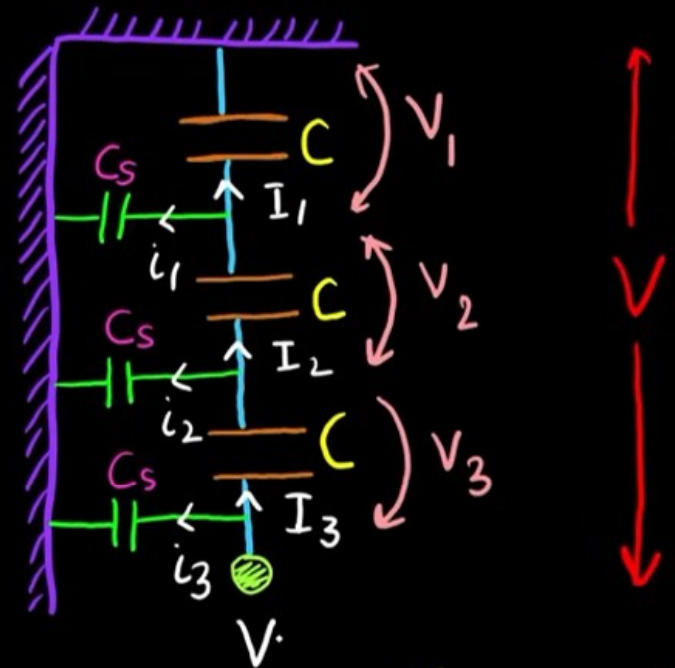

$$V_1 \neq V_2 \neq V_3$$

unequal  
voltage  
distribution

# # String Efficiency

"This unequal distribution of voltage is expressed in terms of string  $\eta$ "


$$\text{String } \eta = \frac{\text{Voltage across the string}}{n \times \text{voltage across disc nearest to conductor}} \times 100$$

$$\text{String } \eta = \frac{V}{n \times V_3} \times 100$$

$V \rightarrow$  phase voltage

$n \rightarrow$  no. of disc in string
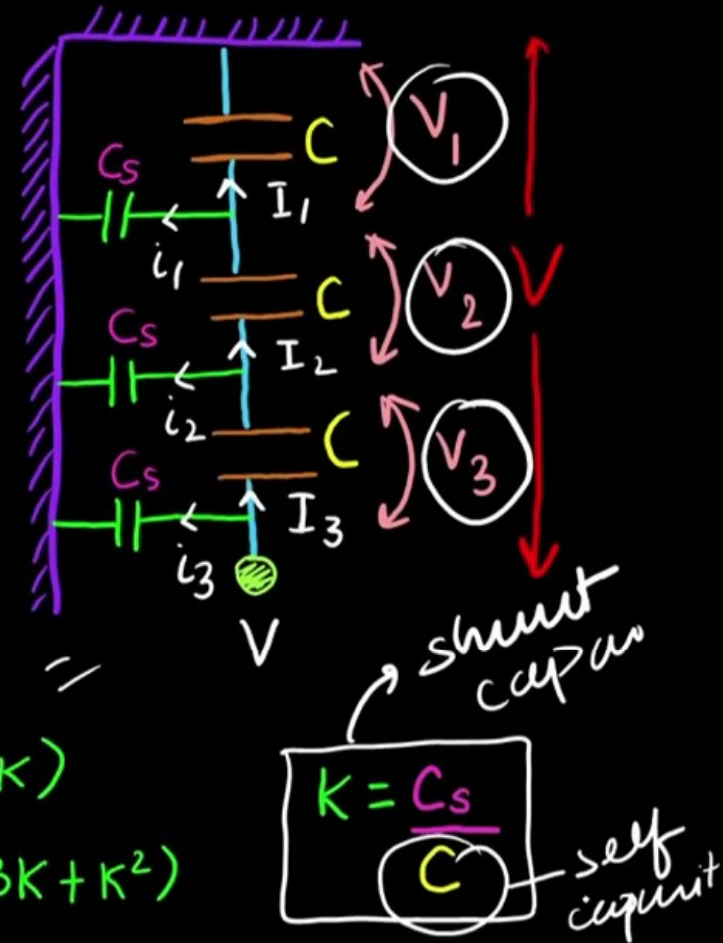
$$\begin{aligned} V_1 &= V_1 \\ V_2 &= V_1(1+K) \\ V_3 &= V_1(1+3K+K^2) \\ V &= V_1 + V_2 + V_3 \end{aligned}$$






## # Important Observation

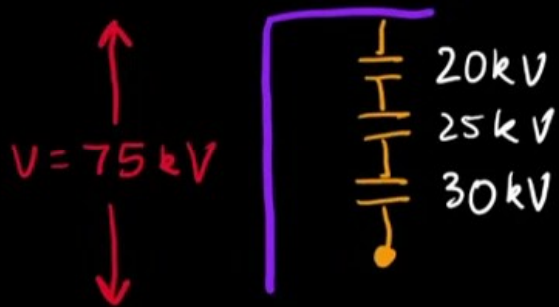
1. If  $V_1 = V_2 = V_3$

$$\eta = \frac{V_1 + V_2 + V_3}{n V_3} = \frac{3V_1}{3V_1} = 100\%$$

"Uniform the voltage distribution, greater the string  $\eta$ "



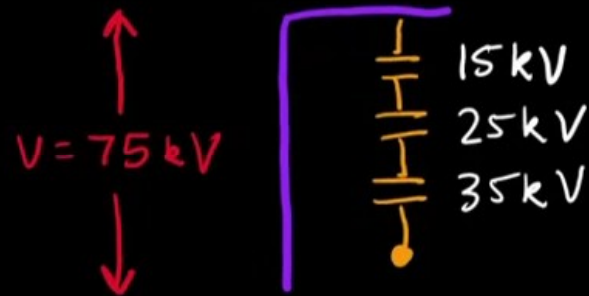
$$\eta = \frac{75 \text{ kV}}{3 \times 30 \text{ kV}} = 83.3\%$$



$$\eta = \frac{75 \text{ kV}}{3 \times 35 \text{ kV}} = 71.4\%$$

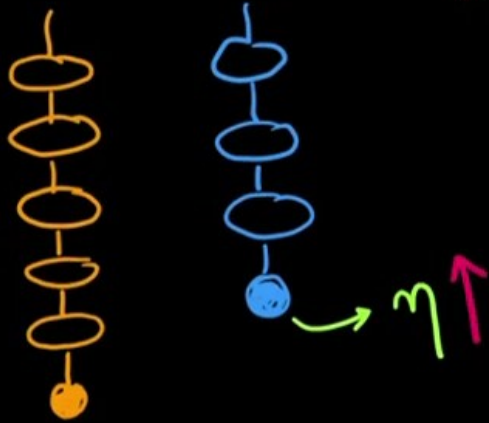2. String  $\eta \propto \frac{1}{\text{no. of disc}}$



"Larger the no. of disc used in string, higher the non-uniformity in voltage distribution"

3. String  $\eta \propto \frac{1}{V_3} \propto \frac{1}{(1+3K+K^2)}$

uneven  
voltage  
distribution

$$K \uparrow = \frac{C_s}{C} \uparrow$$




"Higher the shunt capacitance,  
Lower the string  $\eta$ "

4. Higher the string  $\eta \longrightarrow$  Better the utilization of Insulator

String  $\eta = 100\%$ .

Equal voltage distribution

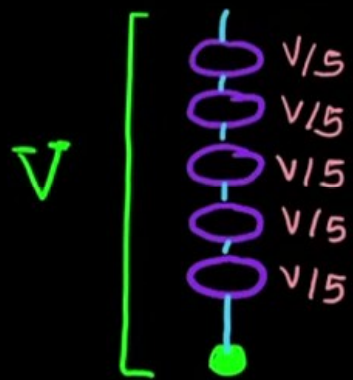


Insulators  
are equally  
utilized

String  $\eta = 70\%$ .

Unequal voltage  
distribution

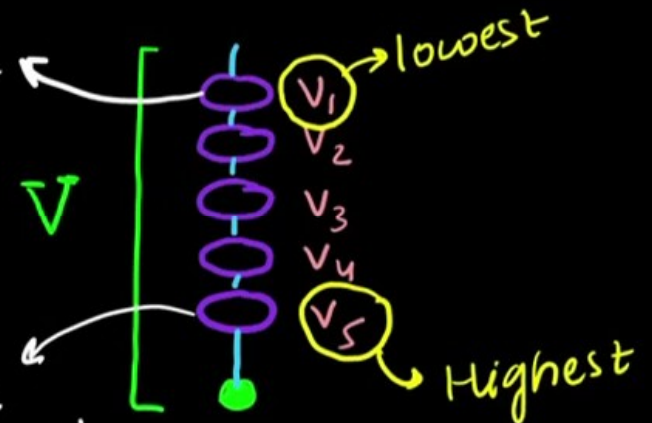under  
utilized  
Under  
loaded or  
less  
stressed



Over  
stressed  
or  
overloaded  
over utilized

5. It is important to improve string  $\eta$

due to shunt capacitance

Unequal distribution of charging current

$$I_3 > I_2 > I_1$$

more likely to be punctured


Maxm voltage across the disc nearest to conductor

$$V_3 > V_2 > V_1$$


unequal voltage distribution





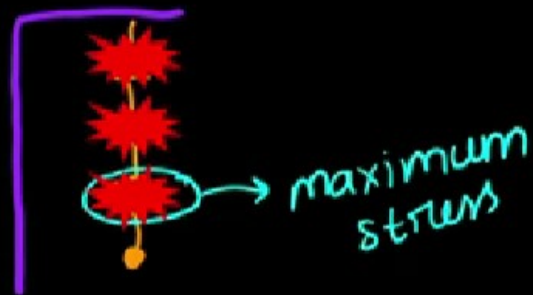

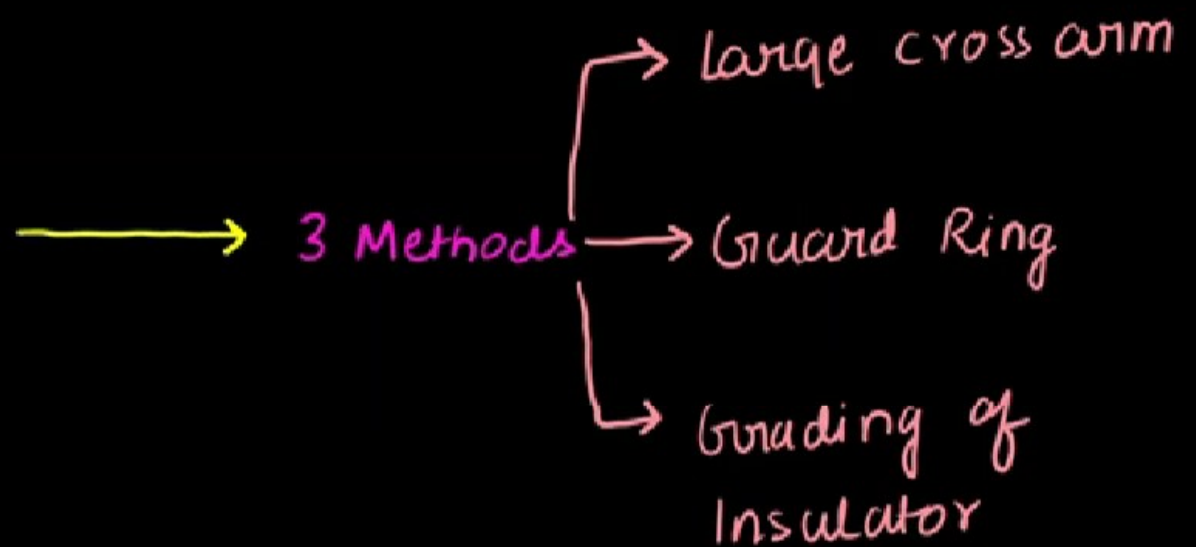"It is important to equalize the voltage stress across each insulator"



# IMPROVING STRING $\eta$



**-Dr. Pranjal Saxena**

(Assistant Professor)

**B.Tech, M.Tech, PhD**

techinsight08@gmail.com




# # Main Culprit of voltage inequality

string  $\eta \propto \frac{1}{V_3} \propto \frac{1}{(1+3K+K^2)}$

$$K = \frac{C_s}{C}$$

main culprit

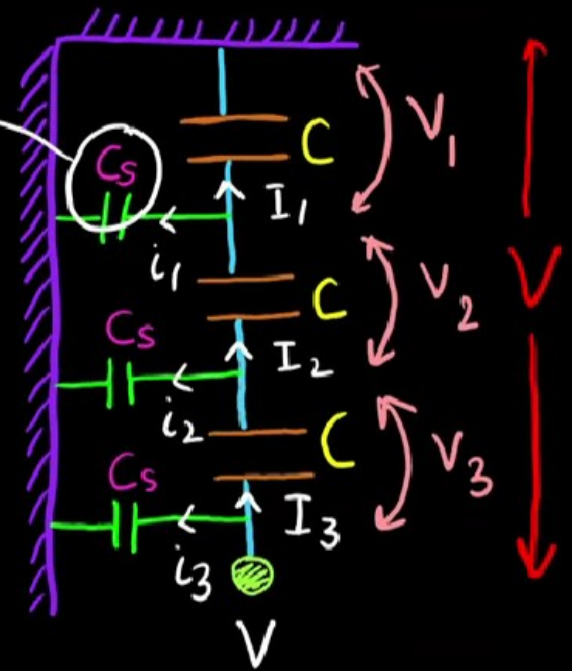



It is important to neutralize  $C_s$

long cross  
ARM

Guard  
Ring

# # Long Cross Arm

$$C_{sh} = \epsilon_0 A \frac{1}{d}$$

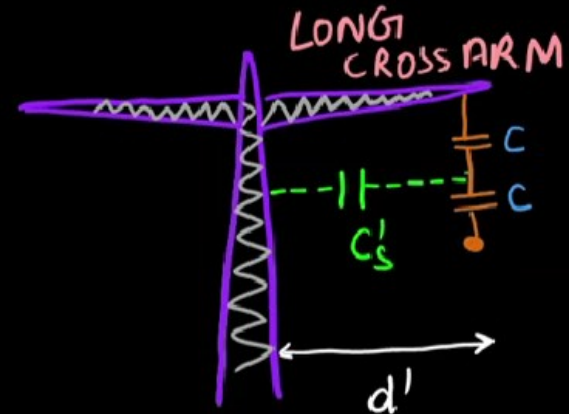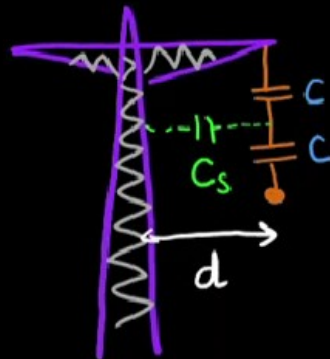

$$d < d'$$

$$C_s > C'_s$$

$K = 0.1$  is limit  $\rightarrow$   $K > K'$   $\rightarrow$  string  $n \uparrow$   
 $\rightarrow$  costly  
 $\rightarrow$  weakens pole strength



# # Guard Ring

$i_2 = i_2'$


$i_1 = i_1'$

adjusted


charging current of  $C_s$

current division

unequal voltage distribution

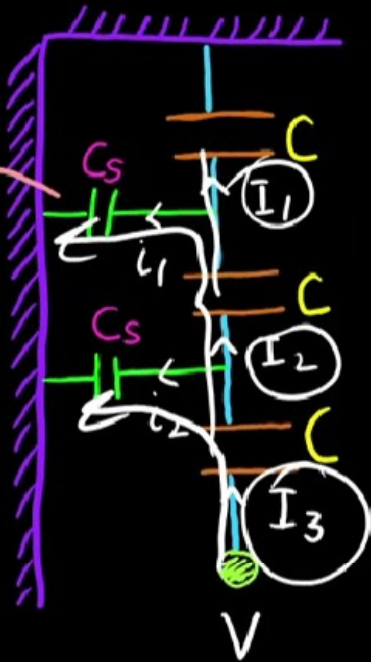

string n Improves

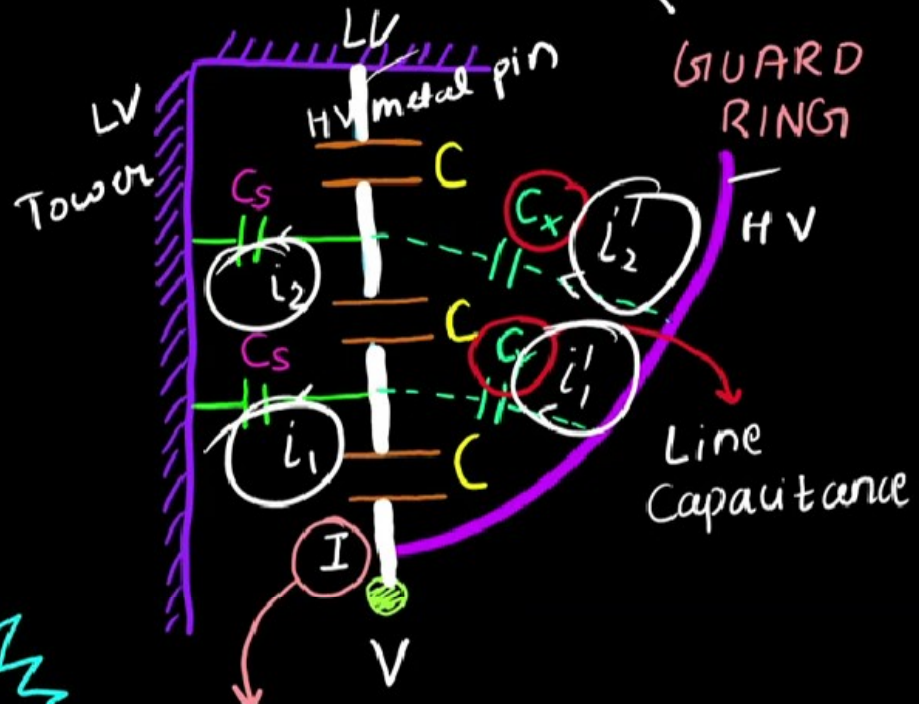

same charging current

Equal voltage distribution




$C$



Self Capacitance



Capacitance of Insulator

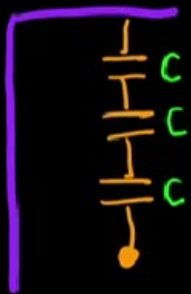


$C_s$



Shunt Capacitance



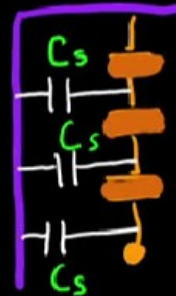
blw Insulator pin and Tower or Insulator disc to Earth




$C_x$




Line Capacitance

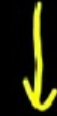

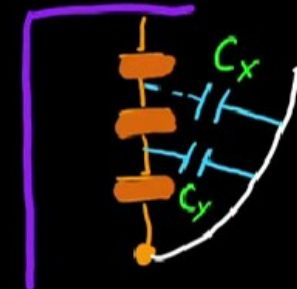blw Insulator pin and line conductor (Guard Ring)





## # Grading of Insulator

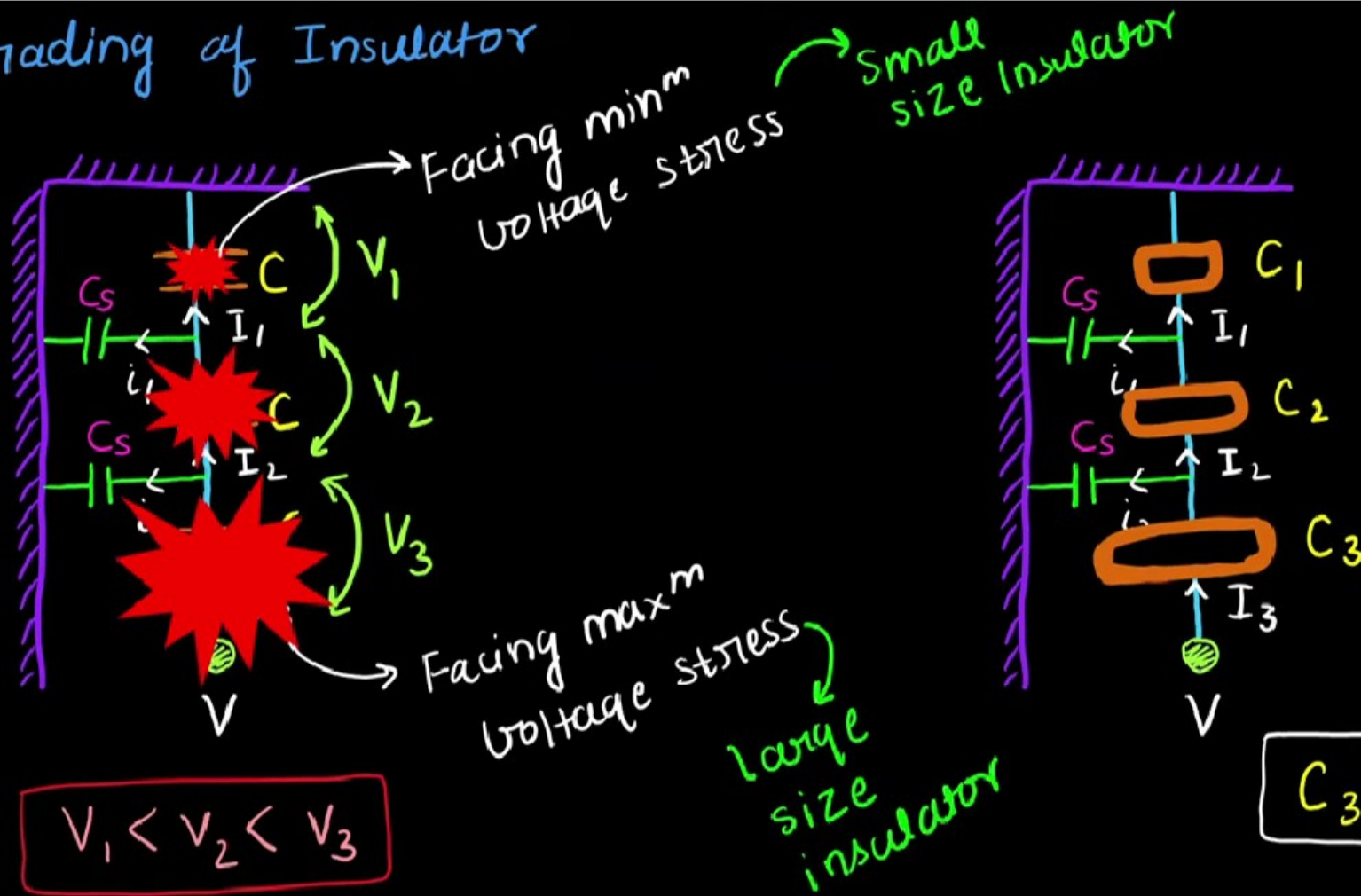

# Disadvantage  $\rightarrow$  Different size insulator required

## # Purpose

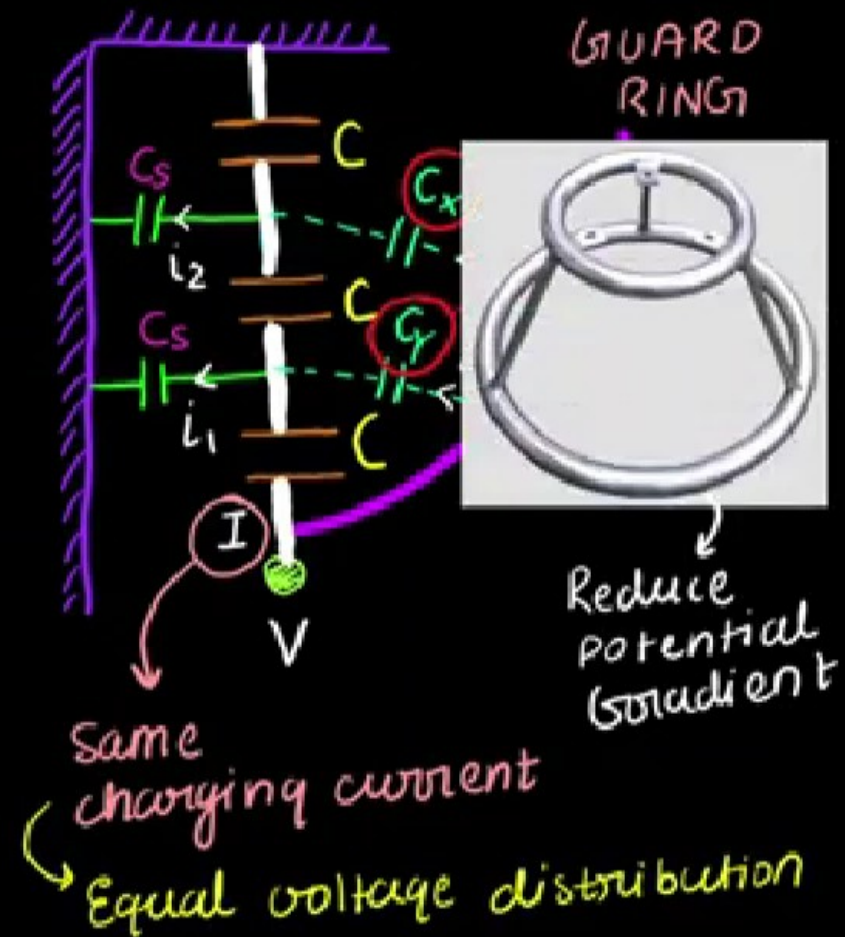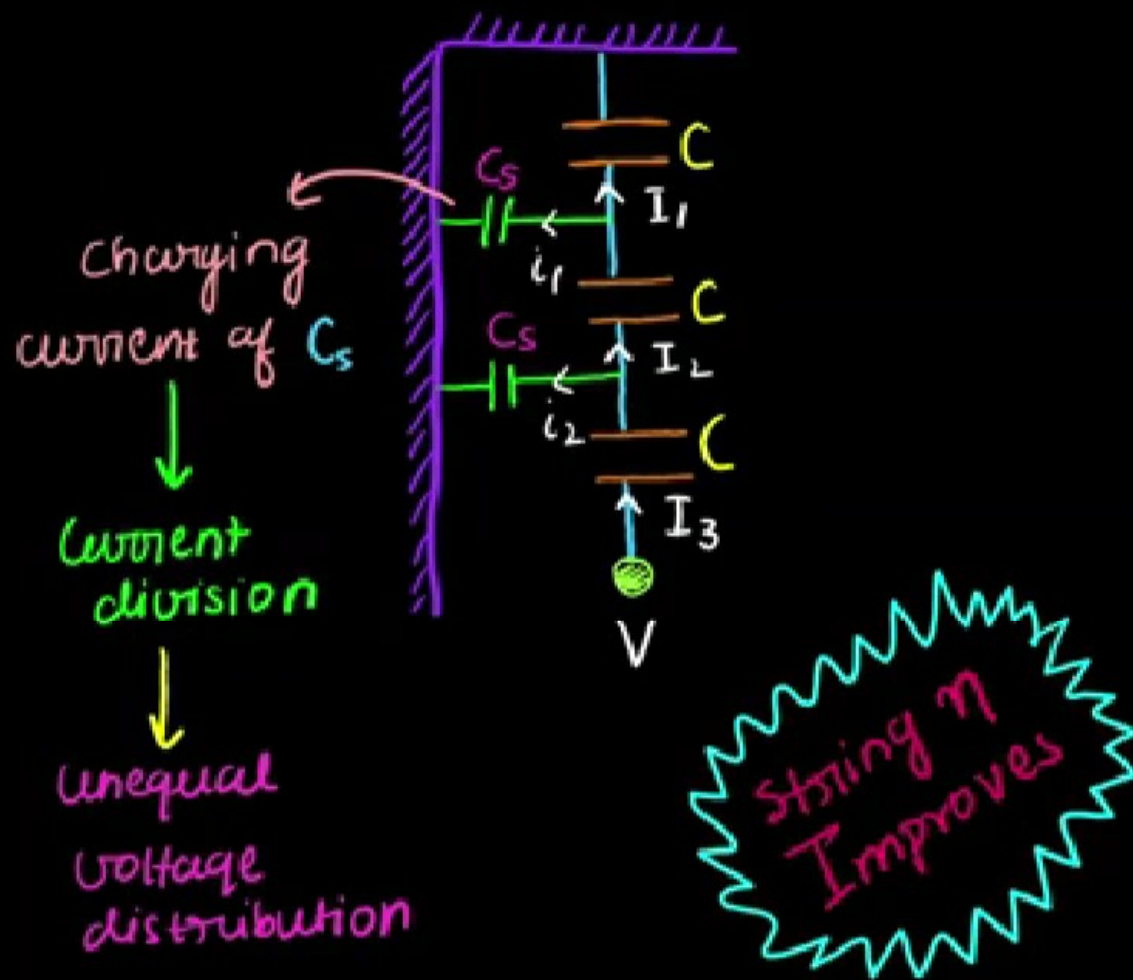



# GRADING RING



**-Dr. Pranjal Saxena**

(Assistant Professor)

**B.Tech, M.Tech, PhD**

techinsight08@gmail.com





## # Grading Ring

"A metal ring that encircles the insulators which are close to conductor"





GRADING RING

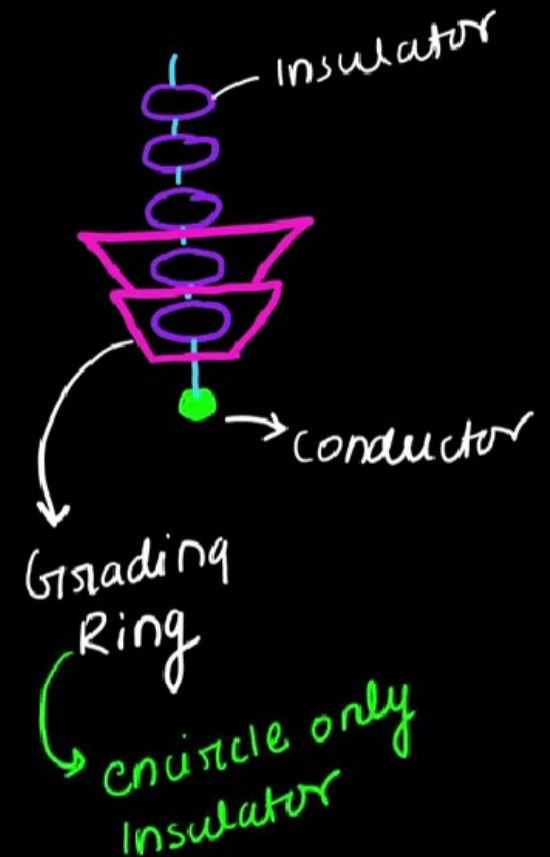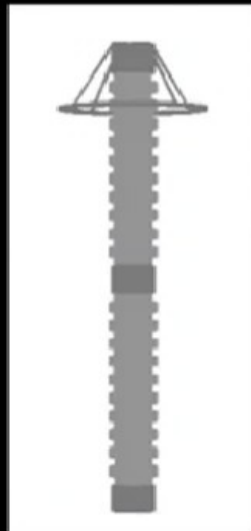


Position → Place near insulator, next to conductor

## # Benefits of Grading Ring

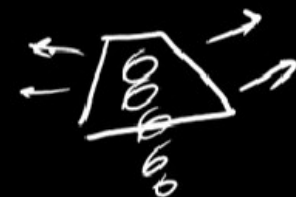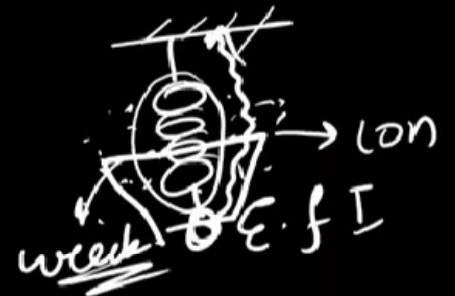1. Reduces voltage gradient at the end insulator, allow the use of cheaper and small size insulator.
2. Improves string efficiency  $\rightarrow$  leads to better utilization of insulators
3. Reduce aging and deterioration of Insulator.
4. Keeps the electric field away from Insulator body, thus prevents flashover.



## # Application

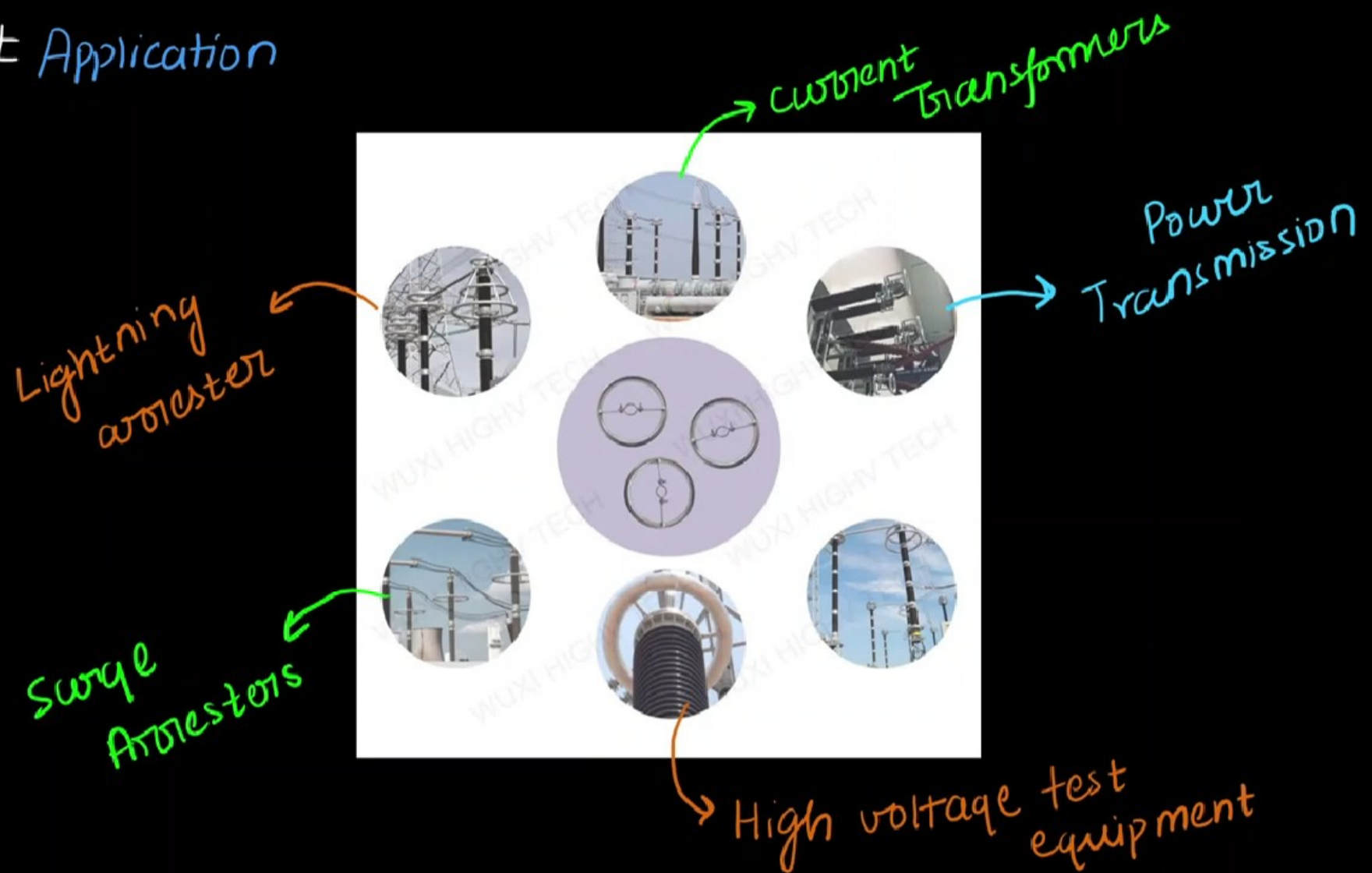



**GRADING  
RING**

Insulator  
life ↑

strings ↑

corona  
discharge ↓

**CORONA  
RING**